

# Mains Dimmers

And how (not) to work with mains voltage

Tim Clark (eclipse)

October 17, 2014

# DMX

- Previous talk on DMX
- Now I've made the other end
- A mains dimmer

# Background Approach


- BIG potentiometer (used to work that way)
- Instead we slice the waveform
- TRIAC work for this

# TRIAC


- TRIACs are (essentially) 2 back to back thyristors
- Turns on when triggered
- Turns off only when supply hits 0v (ish)
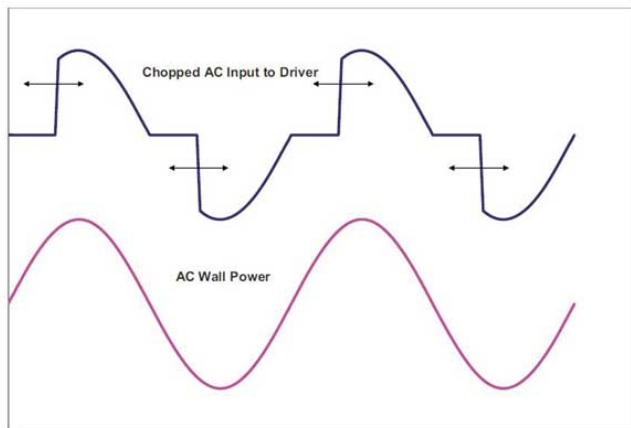
# Waveform Slicing

- Mains hits 0v 100 times a seconds (twice a cycle)
- Detect the 0 cross and time as far as you need



# Waveform Slicing

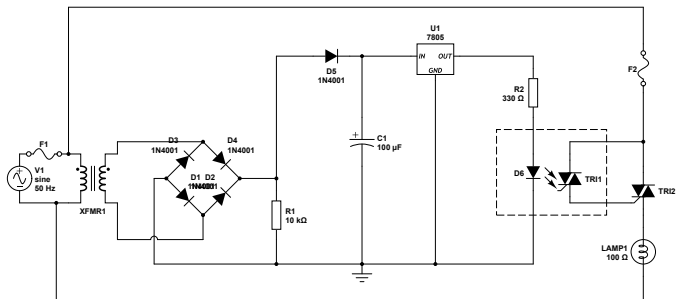

# The Internet

Slides Available at <http://sucs.org/~eclipse>

# Questions?

Any Questions?